

Introduction to HDL

Exam questions

8-Bit 1-8 Demultiplexer

Problem

Design a 1-to-8 Demultiplexer that accepts an 8-bit wide input to an 8-bit wide output.

Simplified Diagram

8-Channel (8-to-1) Demultiplexer

