

Introduction to HDL

Exam questions

8-bit 8-to-1 Multiplexer

Problem

Design an 8-to-1 Multiplexer that accepts 8-bit wide inputs to an 8-bit wide output.

Simplified Diagram

8-Channel (8-to-1) Multiplexer

