

Introduction to HDL

Exam questions

64-bit number parity checker

Problem

Design a combinational circuit that checks whether a number is even or odd. There's only one input 'A' and one output 'isEven'. If isEven=1 then 'A' is even.

Simplified Diagram

64-bit number parity checker diagram

